

13. Oszillatoren. 正弦波振荡器.



基本原理.

设开环放大倍数 $K(s) = \frac{U_0(s)}{U_i(s)}$, 反馈系数 $F(s) = \frac{U_f(s)}{U_0(s)}$, 闭环 $K_{cl}(s) = \frac{U_0(s)}{U_s(s)}$

$U_i(s) = U_s(s) + U_f(s) \Rightarrow U_s(s) = U_i(s) - U_f(s)$

$K_{cl}(s) = \frac{U_0}{U_i - U_i F(s)} = \frac{U_0/U_i}{1 - \frac{U_f U_0}{U_i U_0}} = \frac{K(s)}{1 - F(s) \cdot K(s)} \Rightarrow$ 自激振荡 $F(s)K(s) = 1$. 则没有输入电路也能振荡.

Beispielerschaltung

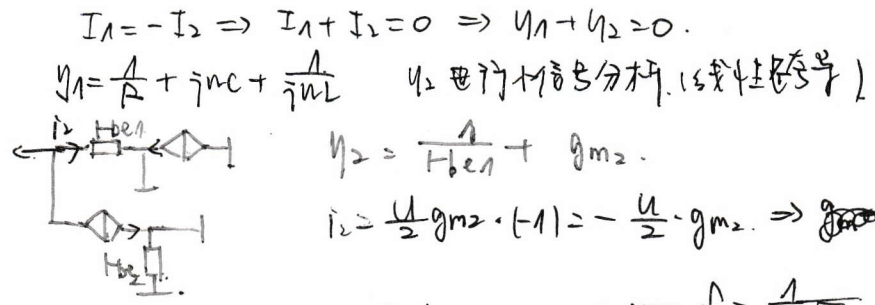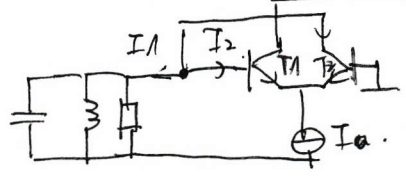

$I_1 = -I_2 \Rightarrow I_1 + I_2 = 0 \Rightarrow U_1 + U_2 = 0$

$Y_1 = \frac{1}{R} + j\omega C + \frac{1}{j\omega L}$ U_2 进行信号分析 (线性电路)

$Y_2 = \frac{1}{j\omega L} + g_{m2}$

$i_2 = \frac{U_2}{j\omega L} \cdot (-1) = -\frac{U_2}{j\omega L} \cdot g_{m2} \Rightarrow Y_2 = -\frac{g_{m2}}{j\omega L} = \frac{jg_{m2}}{\omega L}$

$\Rightarrow \frac{1}{R} = \frac{I_0}{4U_T}, I_0 = \frac{4U_T}{R}, j\omega C + \frac{1}{j\omega L} = 0 \Rightarrow -\omega^2 CL + 1 = 0 \Rightarrow \omega = \frac{1}{\sqrt{2\pi LC}}$

非线性分析. 由路方程

$I_1 = \frac{U}{R} + \frac{1}{L} \int u dt + C \frac{du}{dt}$ $I_2 = \frac{I_0}{2} (1 - \tanh \frac{u}{2U_T})$

$\Rightarrow I_1 + I_2 = 0, \frac{dI_1}{dt} + \frac{dI_2}{dt} = 0 \Rightarrow 0 = \frac{1}{R} \frac{du}{dt} + \frac{1}{L} u + C \frac{d^2 u}{dt^2} - \frac{I_0}{4U_T} (1 - \tanh^2 \frac{u}{2U_T}) \frac{du}{dt}$

$\Rightarrow u + \frac{L}{R} [1 - \frac{I_0 R}{4U_T} (1 - \tanh^2 (\frac{u}{2U_T}))] \frac{du}{dt} + LC \frac{d^2 u}{dt^2} = 0$

$\Rightarrow \frac{d^2 u}{dt^2} + \frac{1}{RC} [1 - \frac{I_0 R}{4U_T} (1 - \tanh^2 (\frac{u}{2U_T}))] \frac{du}{dt} + \frac{1}{LC} u = 0$

产生正弦振荡. $u = A \cos \omega t, \dot{u} = -A \omega \sin \omega t \Rightarrow c_1 e^{j\omega t} + c_2 e^{-j\omega t}$. 其中 $1 - \frac{I_0 R}{4U_T} [1 - \tanh^2 (\frac{u}{2U_T})] = 0$

$\begin{cases} 0 = \tanh^2 (\frac{u}{2U_T}) \\ 1 = \frac{I_0 R}{4U_T} \end{cases} \Rightarrow \begin{cases} u = 0 \\ I_0 = 4U_T/R \end{cases}$

$\Rightarrow u = \hat{u}_1 \sin \omega t, f_1 = \frac{1}{2\pi \sqrt{LC}}$

非线性分析. 傅里叶级数 (-阶), $N_1(j\omega)$, 非线性元件的跨导. G 线性元件的阻抗.

$I_2 = F(u) = -\frac{I_0}{2} (1 - \tanh \frac{\hat{u}_1 \sin \omega t}{2U_T})$, $a_1 = 0, b_1 = -\frac{I_0}{2\pi} \int_0^{2\pi} (1 - \tanh \frac{\hat{u}_1 \sin \omega t}{2U_T}) \sin \omega t dt$

$N_1(j\omega) = \frac{b_1}{\hat{u}_1}, G_1(j\omega) = R + \frac{1}{j\omega C} + j\omega L \Rightarrow \frac{1}{j\omega C} + j\omega L = 0 \Rightarrow f = \frac{1}{2\pi \sqrt{LC}}$

$\Rightarrow \frac{b_1}{\hat{u}_1} \cdot R = 1 \Rightarrow b_1 = \frac{\hat{u}_1}{R} = \frac{I_0}{2\pi} \int_0^{2\pi} \tanh \frac{\hat{u}_1 \sin \omega t}{2U_T} \sin \omega t dt$

$1 = \frac{I_0 \cdot R}{\hat{u}_1} \frac{\hat{u}_1}{2\pi} \int_0^{2\pi} \tanh \frac{\hat{u}_1 \sin \omega t}{2U_T} \sin \omega t dt = \frac{I_0 \cdot R}{2\pi} \int_0^{2\pi} \tanh \frac{\hat{u}_1 \sin \omega t}{2U_T} \sin \omega t dt$

每次 $m=2$ $n=2m$

$\sin^n x = \begin{cases} \frac{2^n - 1}{2^n} \frac{\pi}{2} & n=2m \\ 0 & n=2m+1 \end{cases}$

$\rightarrow \frac{x}{y} \cdot \frac{1}{\pi} \int_0^{2\pi} [\tanh(y \sin a)] \sin a da - 1 = 0$. 其中, $y = \frac{\hat{u}_1}{2U_T}, x = \frac{I_0 R}{4U_T}$


① $\tanh = P$ 阶 (反) $\tanh(x) \approx x \Rightarrow \frac{x}{y} \cdot \frac{1}{\pi} \cdot y \cdot \frac{1}{2} \cdot 2\pi - 1 = 0, x=1, y$ muss klein sein.

② $\tanh = P$ 阶. $\tanh(x) \approx x - \frac{x^3}{3} \Rightarrow \frac{x}{y} \cdot \frac{1}{\pi} \int_0^{2\pi} [y \sin a - \frac{y^3 \sin^3 a}{3}] da = \frac{x}{y} \cdot \frac{1}{\pi} \cdot (y \cdot \pi - \frac{y^3}{3} \cdot \frac{3\pi}{4}) - 1 = 0$

③ $\tanh \approx P$ 阶 $\tanh(x) \approx x - \frac{x^3}{3} + \frac{2x^5}{15}$, $x + x^2 \frac{2x}{3} - \frac{1}{15} \cdot \frac{11}{24} - 1 = 0 \Rightarrow x > 1, x < \frac{16}{13}$

大信号 $\tanh(x) = \pm 1 \Rightarrow \hat{u}_1 = \frac{2}{\pi} \pi I_0$ $I_0 > \frac{4U_T}{R}, \hat{u}_1 = 0, I_0 < \frac{4U_T}{13R} = 42.2 \mu A, \hat{u}_1 = 63.4 mV$

02-01

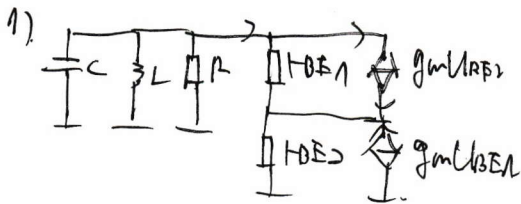

$$g_m = \frac{I_0}{2U_T} \quad U_{BE1} = \frac{U}{2} \quad U_{BE2} = -\frac{U}{2}$$

$$I = \frac{U}{R} = \frac{U}{\frac{2}{g_m} \cdot \frac{I_0}{2}} = \frac{4Ug_m}{I_0} \quad |A| = |1| \Rightarrow I_0 = \frac{4Ug_m}{A} = 34.7 \mu A$$

$$g_m = 0.67 \text{ mS}$$

1) $f_1 = \frac{1}{2\pi\sqrt{LC}} \Rightarrow C = 2.133 \mu F$

02-02

1) $Z = \frac{1}{j\omega C + \frac{1}{j\omega L + \frac{1}{j\omega C} + R}}$, cp renläsning $Z = j\omega L + \frac{1}{j\omega C} + R$ cp-beräkning för resonansfrekvens

$$f_0 = \frac{1}{2\pi\sqrt{LC}} = 100.32 \text{ kHz} \quad Q = \frac{\omega_0 L}{R} = \frac{1}{R} \cdot \frac{L}{\omega_0} = \frac{L}{R\sqrt{LC}} = \frac{1}{R} \cdot \sqrt{\frac{L}{C}} = 11.1$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad \text{#} \text{ } \omega_0 = \frac{1}{\sqrt{LC}} \cdot \frac{1}{\sqrt{LC}} = \frac{1}{LC}$$

2) $U_a = I_D \cdot R_D + U_{ref}$

$$I_D = (U_2 - I_D \cdot R_S) \parallel Z \parallel g_m \quad Z_S = \frac{1}{R_S + j\omega L + \frac{1}{j\omega C} + R}$$

$$\Rightarrow U_2 = \frac{I_D (R_S + 1)}{g_m} \quad U_a = U_2 \cdot \frac{g_m R_D}{g_m Z_S + 1} + U_{ref} \Rightarrow V \frac{g_m R_D}{g_m Z_S + 1} + \frac{U_{ref}}{U_2}$$

1. Fall $V_1 = 0.367$ 2. Fall $V_2 = 2.11$

3) $k = \frac{U_2}{U_a} = \frac{R_2}{R_1 + R_2} = \frac{1}{1 + \frac{R_1}{R_2}}$

$$V_2 = \frac{U_2}{g_m} \quad V_2 \cdot k \geq 1 \quad \frac{R_1}{R_2} + 1 = V_2 \quad \frac{R_1}{R_2} = V_2 - 1 = 1.11$$

4) $U_a = V_2 \cdot \frac{1}{1 + \frac{R_1}{R_2}} \cdot U_a + U_{ref}$

$$U_{ref} = I_D \cdot R_S = U_a \frac{R_1}{R_1 + R_2} \Rightarrow U_a = I_D \cdot R_S \cdot \left(1 + \frac{R_2}{R_1}\right) = U_a = I_D \cdot R_S \cdot V_2 = 37 \mu V$$

$$U_a - U_{ref} = I_D \cdot R_D \Rightarrow U_{ref} = U_a - I_D \cdot R_D = 1.11 \cdot 37 \mu V = 41 \mu V$$

[Note] U_{ref} is the reference voltage. $U_{ref} = 41 \mu V$ is the reference voltage.

02-03

1) $Y_{11} = \frac{1}{R} + j\omega C + \frac{1}{j\omega L}$ $f_{11} = \frac{1}{2\pi\sqrt{LC}} = 1 \text{ MHz}$ (1000000 Hz)

2) $G(j\omega) = R$ $N(j\omega) = \frac{I_2 \cdot 1}{U} = \frac{-I_0}{2\pi\omega_1} \int_0^{2\pi} \tan^{-1}\left(\frac{\omega_1}{2\omega_T} \cdot \sin m\tau\right) \sin n\tau d\tau$

$$|G(j\omega)| \cdot |N(j\omega)| = 1$$

3) ans Vorlesung

$$\int_0^{2\pi} \sin^n x = \begin{cases} \frac{2m-1}{2m} \cdot \frac{2m-3}{2m-2} \cdot \dots \cdot \frac{1}{2} \cdot 2\pi & n=2m \\ 0 & n=2m-1 \end{cases}$$

3.1) $I_0 = \frac{4U_T}{R} = 34.7 \mu A$

3.2) $U_0 = \frac{4U_T}{\sqrt{1 - \frac{4U_T}{R I_0}}} = 38 \text{ mV}$

3.3) pos. Halbwelle $I_2 = 0$ neg. Halbwelle $I_2 = I_0$

$$\frac{I_0}{2} \Rightarrow I_0 \quad \text{b} \text{ } \frac{I_0}{2} \Rightarrow I_0 \quad \text{b} \text{ } \frac{I_0}{2} \Rightarrow I_0 \quad \text{x} 2$$

$$2 \cdot \frac{x}{y} \cdot \frac{1}{2} \cdot \int_0^{2\pi} \sin^2 \alpha - 1 = 0 \quad y = \frac{4}{\pi} x$$

$$2 \cdot \frac{x}{y} \cdot \frac{2}{\pi} - 1 = 0 \quad x = \frac{I_0 R}{4U_T} \quad y = \frac{I_0}{2U_T} \quad \hat{U}_1 = 2U_T \cdot \frac{I_0 R}{4U_T} = \frac{2I_0 R}{2U_T} = 191 \text{ mV}$$